

Assignment 5

Title: Parity Generator

Problem Statement: Design and Implement Parity Generator using EX-OR

Hardware and Software

Requirements

Theory:


1) What is Parity?

- A term used to specify the number of ones in a digital word.
- There are two types of parity! - even and odd.
- An even parity generator will produce a logic 1 at its output if the data word contains an odd number of ones.
- An odd parity generator will produce a logic 1 at its output if the data word contains an even number of ones.


2) Even/Odd Parity Example

7 bits of data	count of 1-bits	8-bits including parity	
		even	odd
0000000	0	0000000	1000000

2) Parity Generator

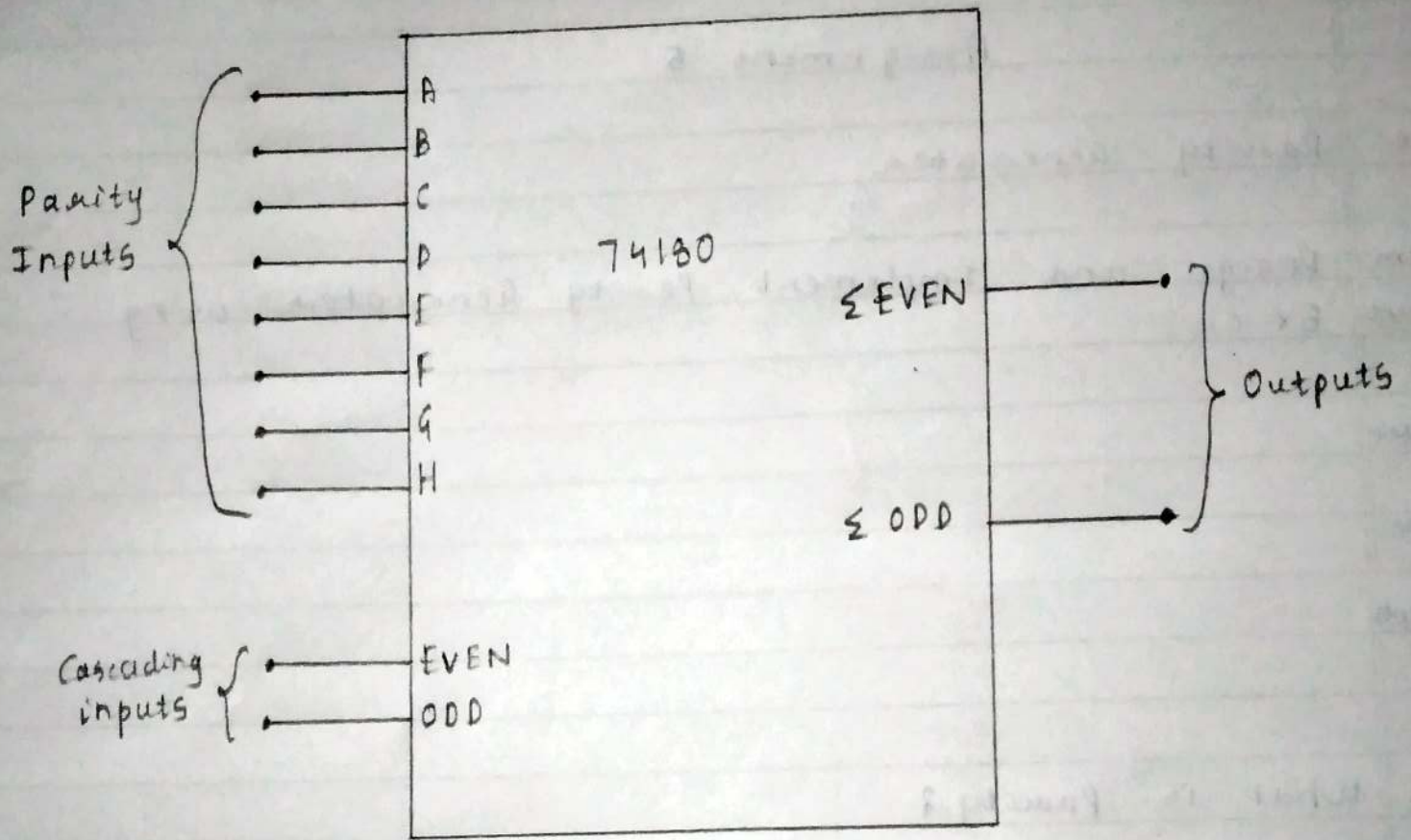

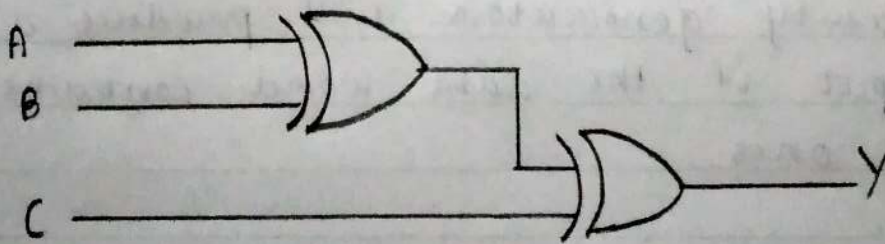→ Circuit diagram (Even parity Generator)



Topic : _____

Design:

1.
 - a. Even Parity Generator
 - Truth table

3-bit message			Even parity bit generator (P)
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


• K-map

		Y			
		BC			
A	\bar{A}	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	A	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
		0	1	0	1
		1	0	1	0
		4	5	7	6

$$\begin{aligned}
 Y &= A\bar{B}\bar{C} + ABC + \bar{A}\bar{B}C + \bar{A}B\bar{C} \\
 &= A(\bar{B}\bar{C} + BC) + \bar{A}(\bar{B}C + B\bar{C}) \\
 &= A(\overline{B \oplus C}) + \bar{A}(B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

SPPU-SE-COMP-CONTENT – KSKA Git

→ Circuit diagram (Even parity detector)

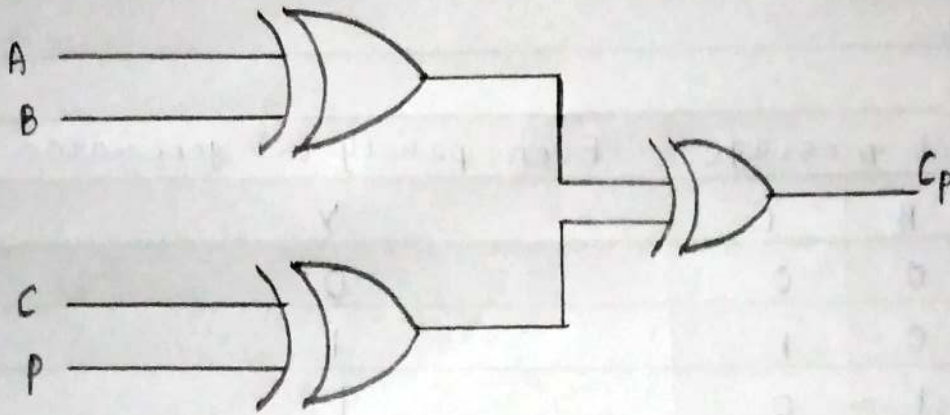

Topic: _____

- b. Even parity checker/detector
- Truth table

4 bit received message				Parity Error
A	B	C	P	Check Cp
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

- K-map


		Cp			
AB	$\bar{C}\bar{P}$	$\bar{C}P$	CP	$C\bar{P}$	
$\bar{A}\bar{B}$	0 ₀	1 ₁	0 ₃	1 ₂	
$\bar{A}B$	1 ₄	0 ₅	1 ₇	0 ₆	
$A\bar{B}$	0 ₁₂	1 ₁₃	0 ₁₅	1 ₁₄	
AB	1 ₈	0 ₉	1 ₁₁	0 ₁₀	

$$\begin{aligned}
 C_p &= \bar{A}\bar{B}\bar{C}P + \bar{A}\bar{B}C\bar{P} + \\
 &\quad \bar{A}B\bar{C}\bar{P} + \bar{A}BCP \\
 &\quad + A\bar{B}\bar{C}P + A\bar{B}C\bar{P} \\
 &\quad + A\bar{B}C\bar{P} + AB\bar{C}P \\
 &= \bar{A}\bar{B}(C\bar{P} + CP) + \\
 &\quad \bar{A}B(C\bar{P} + CP) + \\
 &\quad A\bar{B}(C\bar{P} + CP) + \\
 &\quad AB(C\bar{P} + CP) \\
 &= (C\bar{P} + CP)(\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB) \\
 &= (C\bar{P} + CP)(\bar{A} + A) \\
 &= (C\bar{P} + CP)
 \end{aligned}$$

$$\therefore C_p = A \oplus B \oplus C \oplus P$$

SPPU-SE-COMP-CONTENT KSKA Git

→ Circuit diagram Code Parity Generator

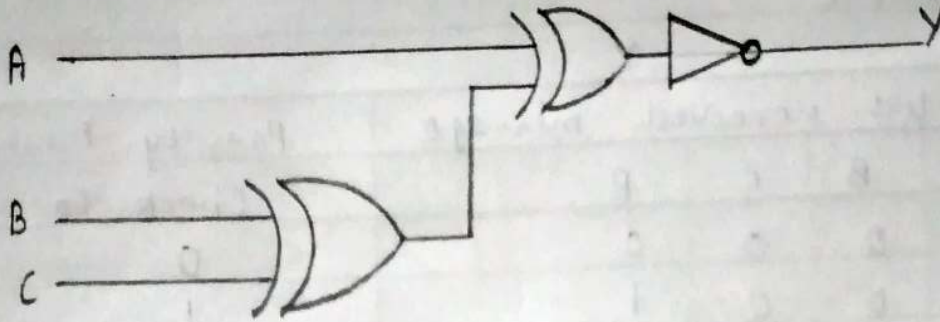

2-a. Odd Parity Generator
• Truth table


3-bit message			Odd Parity bit generator (P)
A	B	C	
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

• K-map Y

		BC			
A		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}		1 ₀	0 ₁	1 ₃	0 ₂
A		0 ₄	1 ₅	0 ₇	1 ₆

$$\begin{aligned}
 Y &= \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + AB\bar{C} \\
 &= \bar{A}(\bar{B}\bar{C} + BC) + A(\bar{B}C + B\bar{C}) \\
 &= \bar{A}(\overline{B \oplus C}) + A(B \oplus C) \\
 &= A \oplus (B \oplus C)
 \end{aligned}$$

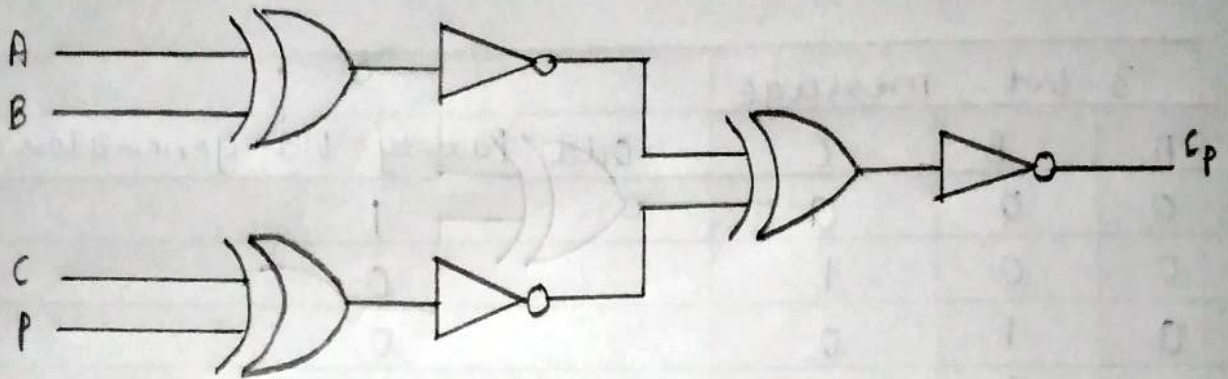→ Circuit Diagram of odd parity generator - KSKA Git



Odd parity Detector

4-bit received message				Parity error check C_p
A	B	C	P	
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

K-map

	C_p	C_p			
AB	\bar{C}_p	C_p	C_p	\bar{C}_p	
$\bar{A}\bar{B}$	1 ₀	0 ₁	1 ₃	0 ₂	
$\bar{A}B$	0 ₄	1 ₅	0 ₇	1 ₆	
AB	1 ₁₂	0 ₁₃	1 ₁₅	0 ₁₄	
$A\bar{B}$	0 ₈	1 ₉	0 ₁₁	1 ₁₀	

$$\begin{aligned}
 C_p &= \bar{A}\bar{B}\bar{C}_p + \bar{A}\bar{B}C_p \\
 &+ \bar{A}B\bar{C}_p + \bar{A}B C_p \\
 &+ A\bar{B}\bar{C}_p + A\bar{B}C_p \\
 &= \bar{A}\bar{B}(\bar{C}_p + C_p) + \bar{A}B(\bar{C}_p + C_p) \\
 &+ A\bar{B}(\bar{C}_p + C_p) + AB(\bar{C}_p + C_p) \\
 &= (\bar{C}_p + C_p)(\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB) \\
 C_p &= (A \oplus B) \oplus (C \oplus P)
 \end{aligned}$$

Conclusion: Designed and Implemented parity Generator using EX-OR. For Educational Use Only