

**SE COMP (2019 Course)  
DIGITAL ELECTRONICS AND LOGIC  
DESIGN**

**MINIMIZATION  
TECHNIQUE  
TOPIC: IC, LOGICAL  
FUNCTION**

# Objectives

- To study pin configuration of logic gates IC
- To study the representation of logical function/Boolean function

Unit I	Minimization Technique	(06 Hours)
Logic Design Minimization Technique -: Minimization of Boolean function using K-map(up to 4 variables) and Quine Mc-Clusky Method, Representation of signed number- sign magnitude representation ,1's complement and 2's complement form (red marked can be removed), Sum of product and Product of sum form, Minimization of SOP and POS using K-map.		
<b>#Exemplar/Case Studies</b>	Digital locks using logic gates	

# INTEGRATED CIRCUIT

- An integrated circuit or monolithic integrated circuit (also referred to as an IC, a chip, or a microchip) is a set of electronic circuits on one small plate ("chip") of **semiconductor material, normally silicon.**
- ICs can be made very compact, having up to several billion transistors and other electronic components in an area the size of a human fingernail.

# INTEGRATED CIRCUIT

## □ LEVEL OF INTEGRATION

### 1.SSI : Small Scale Integration

-It has less than 100 components(about 10gates)

### 2.MSI: Medium Scale Integration

-It contains less than 500 components or have more than 10 but less than 100 gates.


### 3.LSI: Large scale integration

-Number of components is between 500 and 300000 or have more than 100gates.


### 4.VLSI:very large scale integration.

-A process of creating an integrated circuit (IC) by combining thousands of transistors into a single chip. .


# IC:

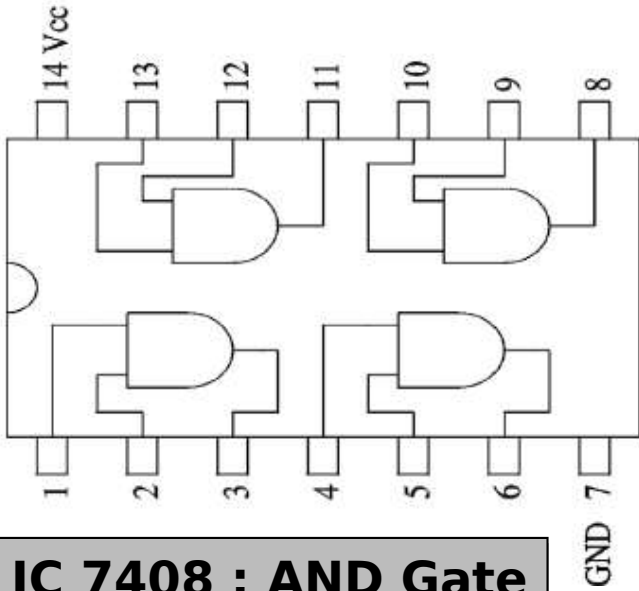

**IC 7408 : AND Gate**

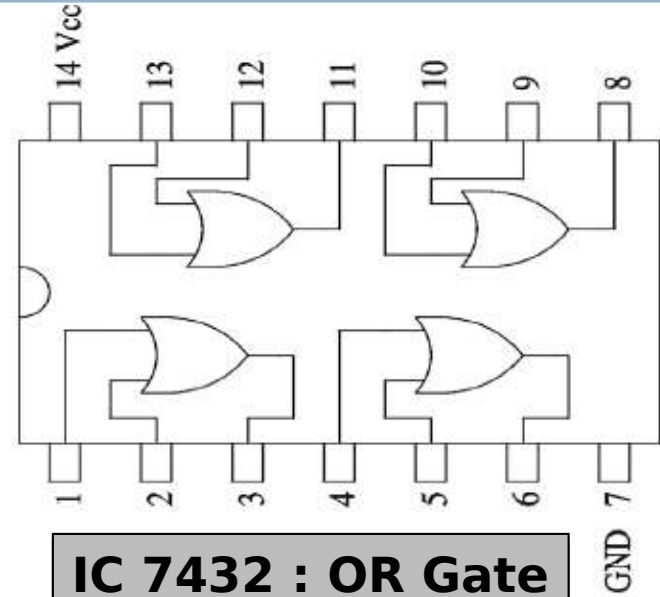


**IC 7432 : OR Gate**

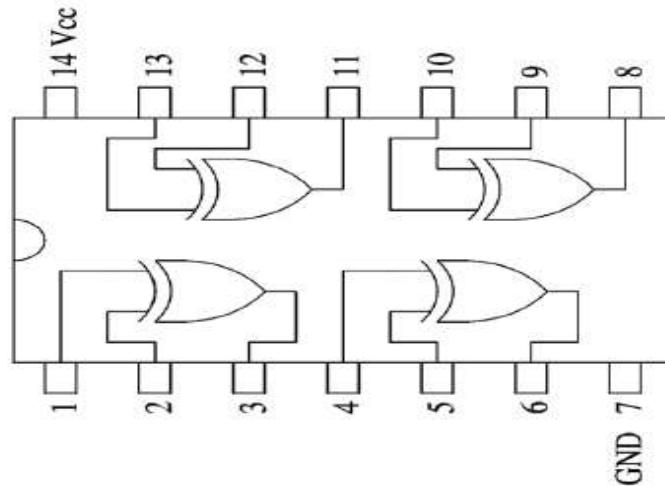


**7486 : Ex-OR Gate**

# IC:

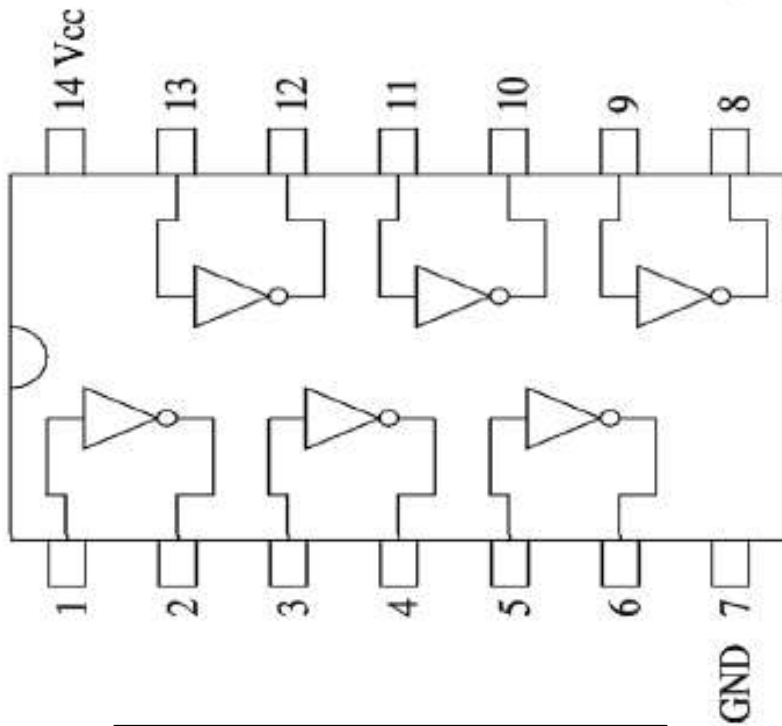

**IC 7404 : NOT Gate**

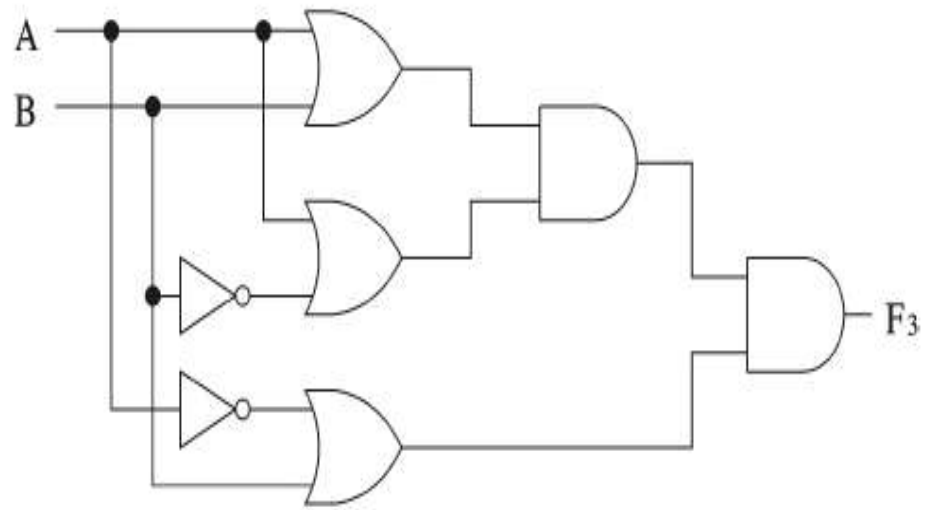


NOT Gate(7404)= 1

AND Gate(7408)= 1

OR Gate(7432)= 1

# IC:

**IC 7400 : NAND Gate = Pin configuration is same as AND gate**

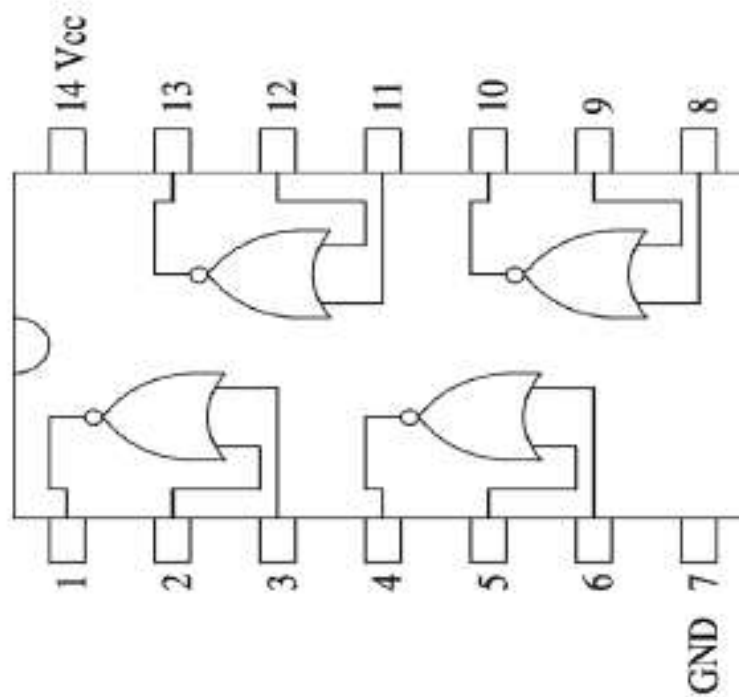

**IC 7402 : NOR Gate**

# Logic Functions

- Logical functions can be expressed in several ways:
  - Truth table
  - Logical expressions
  - Graphical form

Example:

- Majority function
  - ✓ Output is 1 whenever majority of inputs is 1
  - ✓ We use 3-input majority function




# Logic Functions (cont.)

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Logical expression form


$$F = A B + B C + A C$$

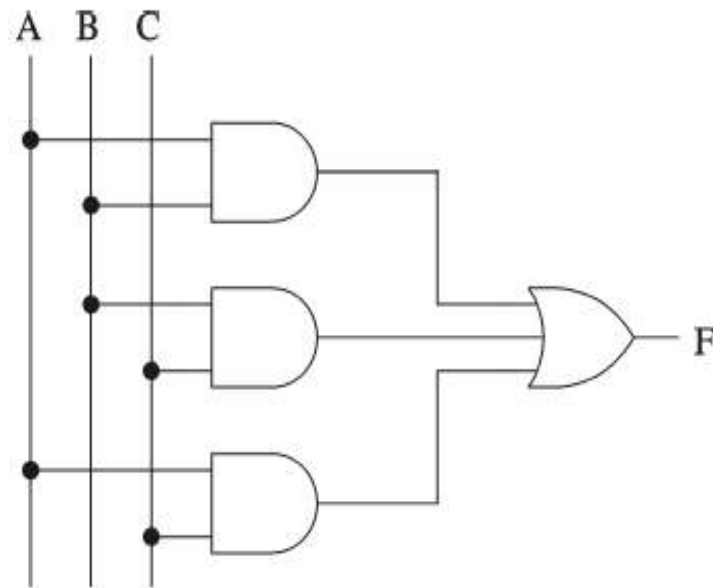


# Logical Equivalence

- All three circuits implement function  $F =$

$A \cdot B$

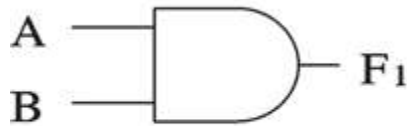


(a)

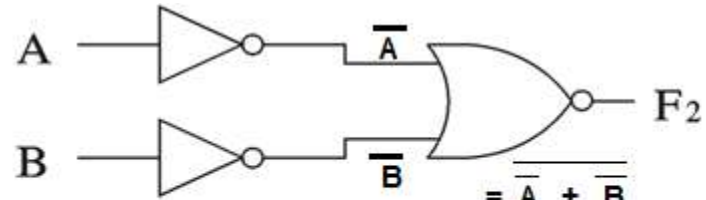

(b)

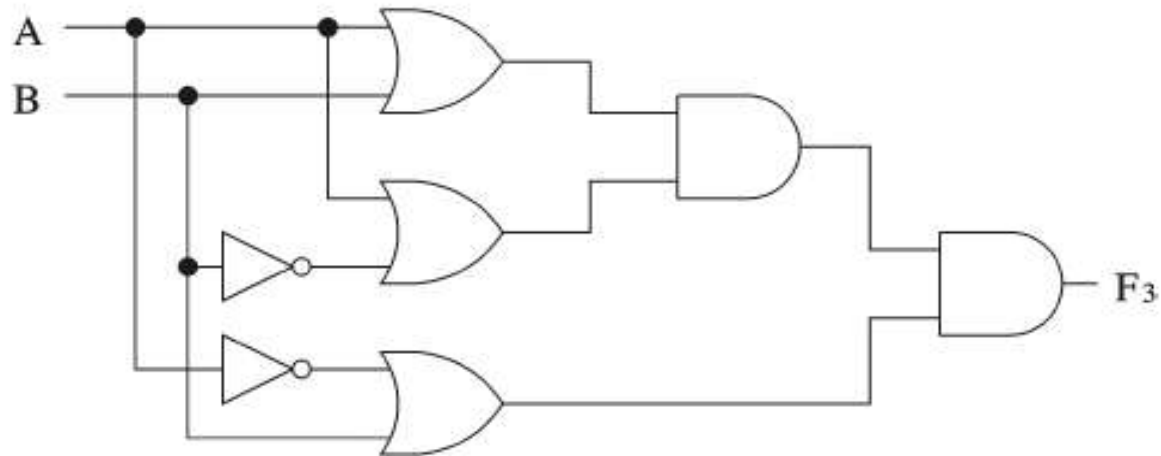
$$\begin{aligned} &= \overline{\overline{A} + \overline{B}} \\ &= \overline{\overline{A}} \cdot \overline{\overline{B}} \\ &= A \cdot B \end{aligned}$$



(c)
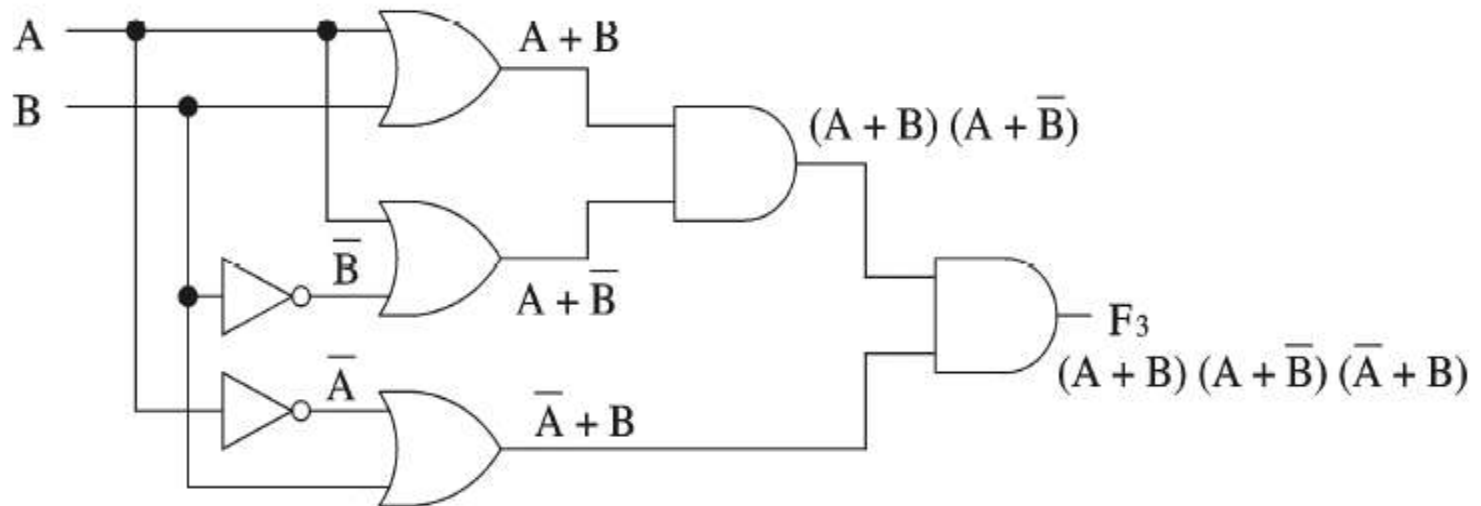
# Logical Equivalence (Cont.)

- Derivation of logical expression from a circuit
  - ✓ Trace from the input to output
    - ✓ Write down intermediate logical expressions



# Logical Equivalence (Cont.)

- Proving logical equivalence: Truth table method

<b>A</b>	<b>B</b>	<b>F1 = A B</b>	<b>F3 = (A + B) (A + <math>\bar{B}</math>) (<math>\bar{A}</math> + B)</b>
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

# How to minimize a Boolean/Logical function?

There are four ways to solve any function.

1. Boolean Algebra.
2. K-Map.
3. Quine-McCluskey Technique.
4. Variable Mapping Function.

# Basic Theorems of Boolean Algebra

## 1. Identity Elements

$$1 \cdot A = A$$

$$0 + A = A$$

## 2. Inverse Elements

$$A \cdot \bar{A} = 0$$

$$A + \bar{A} = 1$$

## 3. Idempotent Laws

$$A + A = A$$

$$A \cdot A = A$$

## 4. Boundness Laws

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

## 5. Distributive Laws

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

## 6. Order Exchange Laws

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

## 7. Absorption Laws

$$A + (A \cdot B) = A$$

$$A \cdot (A + B) = A$$

## 8. Associative Laws

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

## 9. Elimination Laws

$$A + (\bar{A} \cdot B) = A + B$$

$$A \cdot (\bar{A} + B) = A \cdot B$$

## 10. De Morgan Theorem

$$\overline{(A + B)} = \bar{A} \cdot \bar{B}$$

$$\overline{(A \cdot B)} = \bar{A} + \bar{B}$$