

# SPPU-SE-COMP-CONTENT – KSKA Git

Total No. of Questions : 6]

SEAT No. :

**PA-24**

[Total No. of Pages : 2

**[5931]- 34**

**S.E. (Computer Engineering)**

**DIGITAL ELECTRONICS AND LOGIC DESIGN**

**(2019 Pattern) (Semester - I) (210245)**

**Time : 1 Hour**

**[Max. Marks : 30**

**Instructions to the candidates :**

- 1) Attempt Q.1 or Q.2, Q.3 or Q.4., Q.5 or Q.6.
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) Assume suitable data if necessary.

- Q1) a)** Simplify the expression  $F(A,B,C,D) = \sum m(3,4,5,7,9,13,14,15)$  using the K-map method. [5]
- b)** Simplify the expression  $F(A,B,C,D) = \pi M(0,1,4,5,6,8,9,12,13,14)$  using the K-map method. [5]

**OR**

- Q2) a)** Simplify the following logic function using the Quine-McCluskey minimization technique. [8]
- $$Y(A,B,C,D) = \sum m(0,1,3,7,8,9,11,15).$$
- b)** Express the function  $Y = AB+ACD$  in canonical sum of product form. [2]

- Q3) a)** Implement the following Boolean function using 8 : 1 multiplexer [5]
- $$F(A,B,C,D) = \sum m(2,4,5,7,10,14).$$
- b)** Design 4 bit binary to gray code converter circuit using logic gates. [5]

**OR**

- Q4) a)** Explain the rules for BCD addition with suitable example and Design one digit BCD adder using IC 7483. [5]
- b)** How will you implement full adder using half adder? Explain with circuit diagram. [5]

**P.T.O.**

# SPPU-SE-COMP-CONTENT – KSKA Git

- Q5)** a) Explain look Ahead carry generator in detail. [5]  
b) Simplify the expression  $F(A,B,C,D) = \sum m(1,3,7,11,15) + d(0,2,5)$  using the K-map method. [5]

OR

- Q6)** a) What do you mean by parity? Design 3 bit parity generator circuit using even parity bit. [5]  
b) Minimize the following expression using the K-map with minimum hardware. [5]

$$Y = \sum m(1,5,6,7,11,12,13,15)$$

