

Assignment no-1  
SPPU-SE-COMP-CONTENT - KSKA Git


Title: Full Adder and Full Subtractor

Problem Statement: Realize Full Adder and Subtractor Using  
a) Basic Gates and b) Universal gates


Hardware and Software Requirements: Digital Trainer kit, IC 7404, IC 7432, IC 7408, IC 7400, IC 7402, Patch Cord, +5V Power Supply

Theory: Full Adder: (with block diagram)  
Full Subtractor: (with block diagram)  
Universal Gates

# SPPU-SE-COMP-CONTENT – KSKA Git

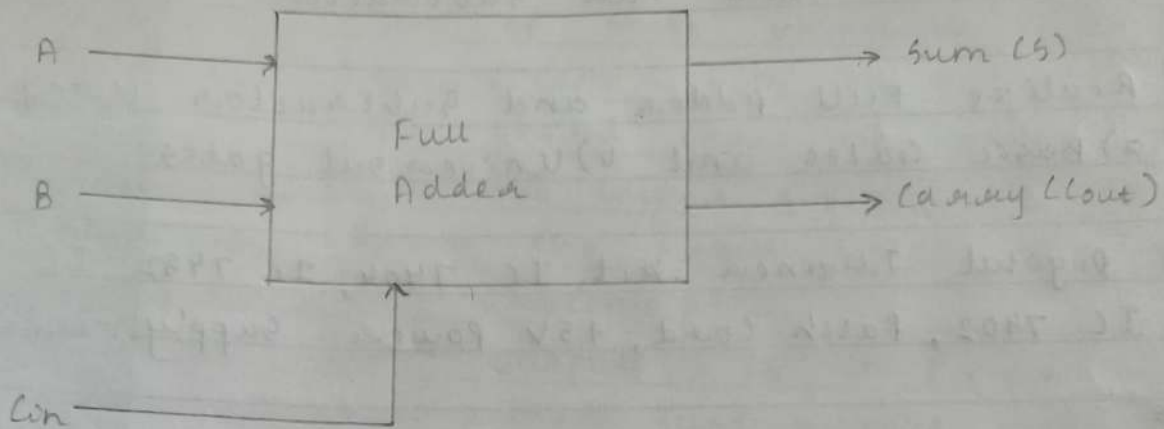

Block diagram of Full Adder

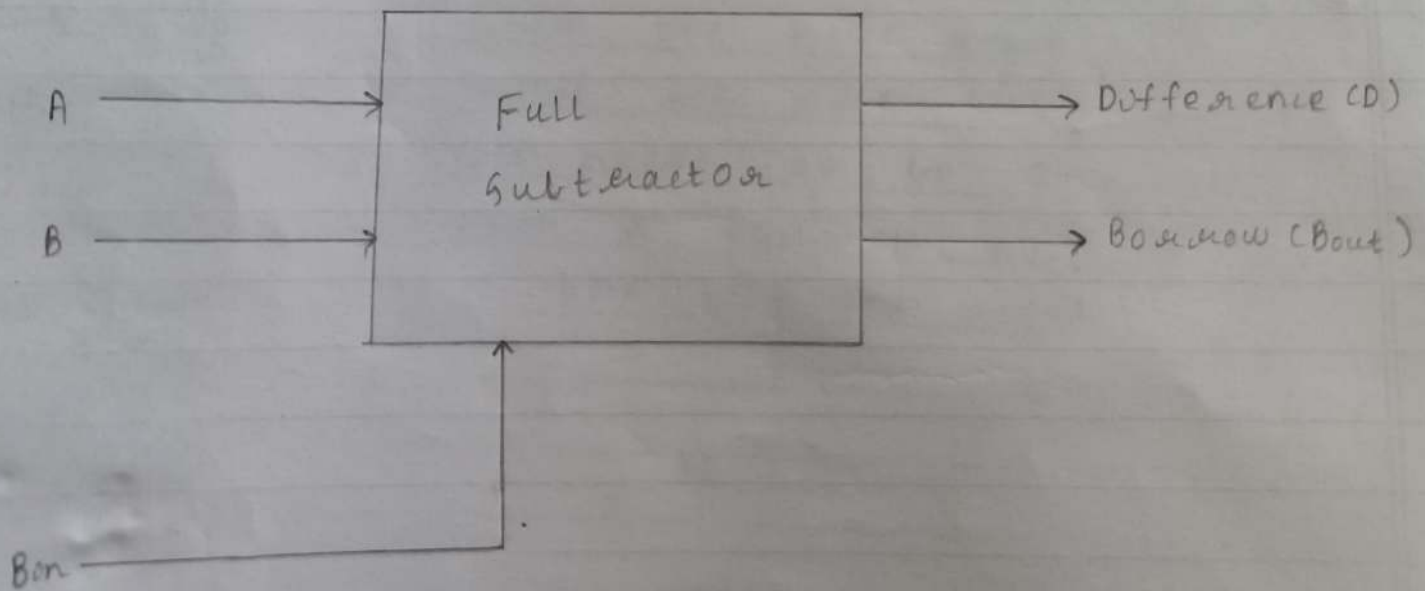

Block diagram of Full Subtractor

# SPPU-SE-COMP-CONTENT - KSKA Git

→ Full Adder:-


- A full adder is a combinational logic circuit that has 3 inputs  $A, B$  and  $C_{in}$  and 2 outputs  $S_{um}$  and  $C_{arry}$  ( $C_{out}$ ).
- Two of these variables  $A, B$  represent the two significant bits to be added.
- The third input represents the carry from previous lower significant position.
- From the truth table, the full adder logic can be implemented.
- The output  $S$  is an Ex-or between the input  $A$  and half-adder sum output with  $B$  and  $C_{in}$  inputs.
- $C_{out}$  will only be true if any of the two inputs out of the three are HIGH.

→ Full Subtractor:-


- A full subtractor is a combinational logic circuit with 3 inputs  $A, B$  and  $B_{in}$  and 2 outputs difference and  $B_{orrow}$  ( $B_{out}$ ).
- Like the half subtractor, the full subtractor generates a borrow out when it needs to borrow from the next digit.
- Since we are subtracting by and, a borrow out needs to be generated when a borrow
- when a borrow out is generated, 2 is added in the current digit.

# SPPU-SE-COMP-CONTENT – KSKA Git

→ Universal Gates

 

NAND Gate

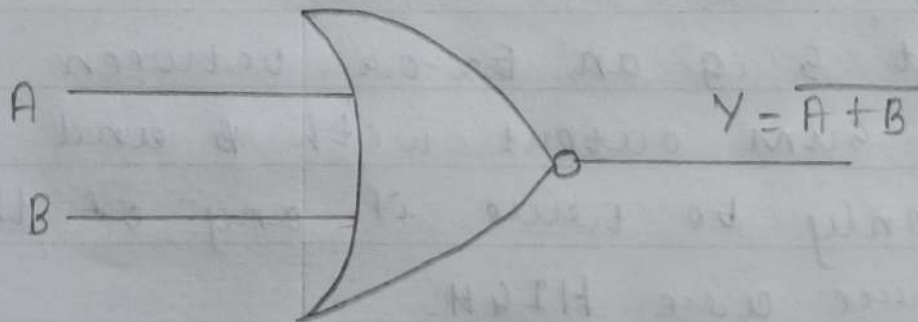

NOR Gate

# SPPU-SE-COMP-CONTENT - KSKA Git

Universal gates:-

A universal gate is a gate which can implement any boolean function without need to use any other gate type.

The NAND and NOR gates are universal gates.

In practice, this is advantageous since NAND and NOR gates are economical and easier to fabricate and are the basic gates used in all IC digital logic families.

# SPPU-SE-COMP-CONTENT - KSKA Git

→ Design:-

1. Full Adder
- Truth table

A	B	cin	S (sum)	cout (Carry)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

• K-map


i) Sum

		B cin			
		$\bar{B} \bar{c}_{in}$	$\bar{B} c_{in}$	$B c_{in}$	$B \bar{c}_{in}$
A	$\bar{A}$	0	1	0	1
	A	1	0	1	0
		0	1	3	2
		4	5	7	6


$$\begin{aligned}
 \text{Sum (S)} &= A \bar{B} \bar{c}_{in} + \bar{A} \bar{B} c_{in} + A B c_{in} + \bar{A} B \bar{c}_{in} \\
 &= \bar{B} (A \bar{c}_{in} + \bar{A} c_{in}) + B (A c_{in} + \bar{A} \bar{c}_{in}) \\
 &= \bar{B} (A \oplus c_{in}) + B (\overline{A \oplus c_{in}}) \\
 &= B \oplus (A \oplus c_{in}) \\
 S &= A \oplus B \oplus c_{in}
 \end{aligned}$$

# SPPU-SE-COMP-CONTENT - KSKA Git

→ Circuit diagram  
1) Using AND Gate

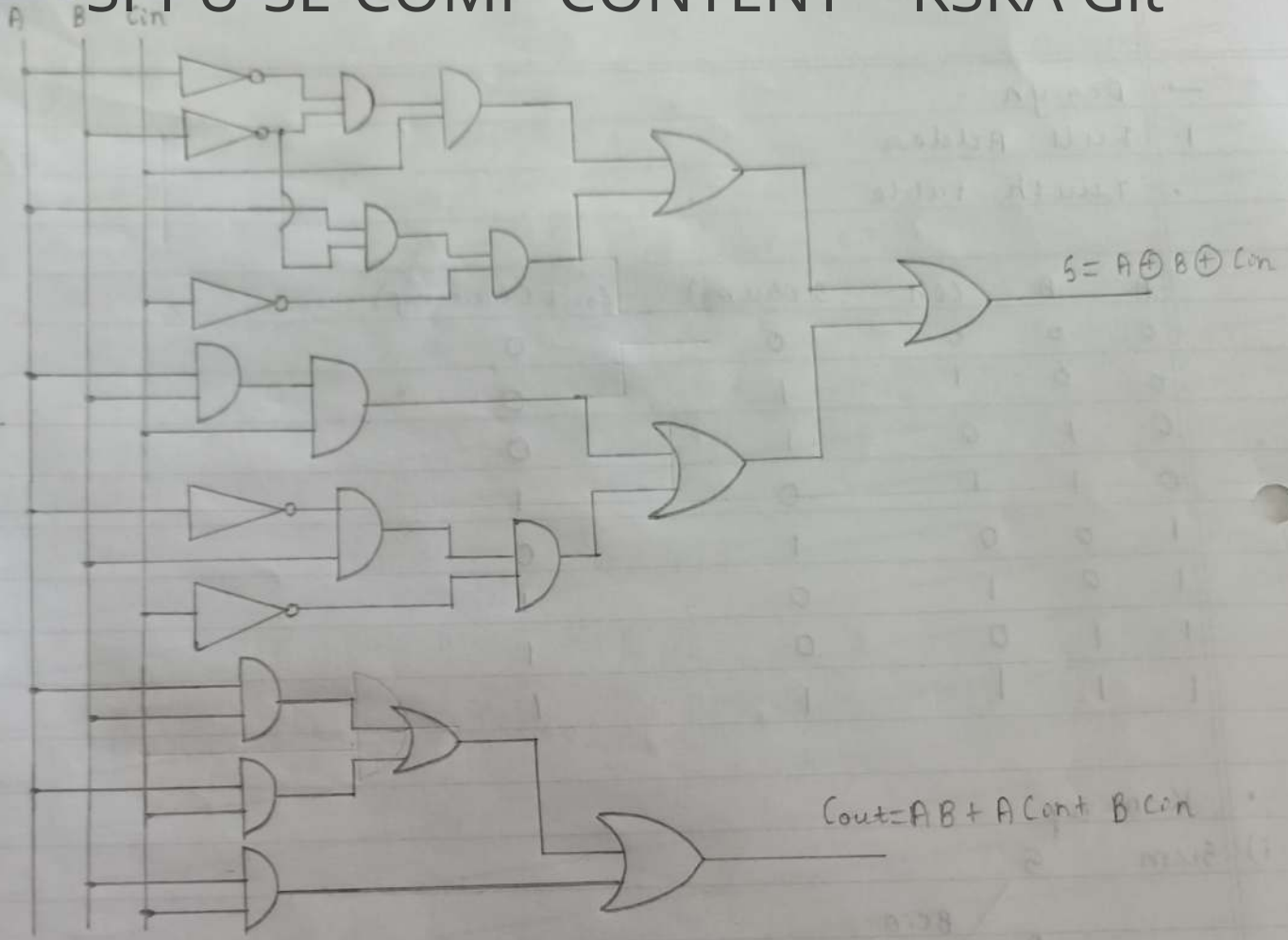

2) Using NAND Gate

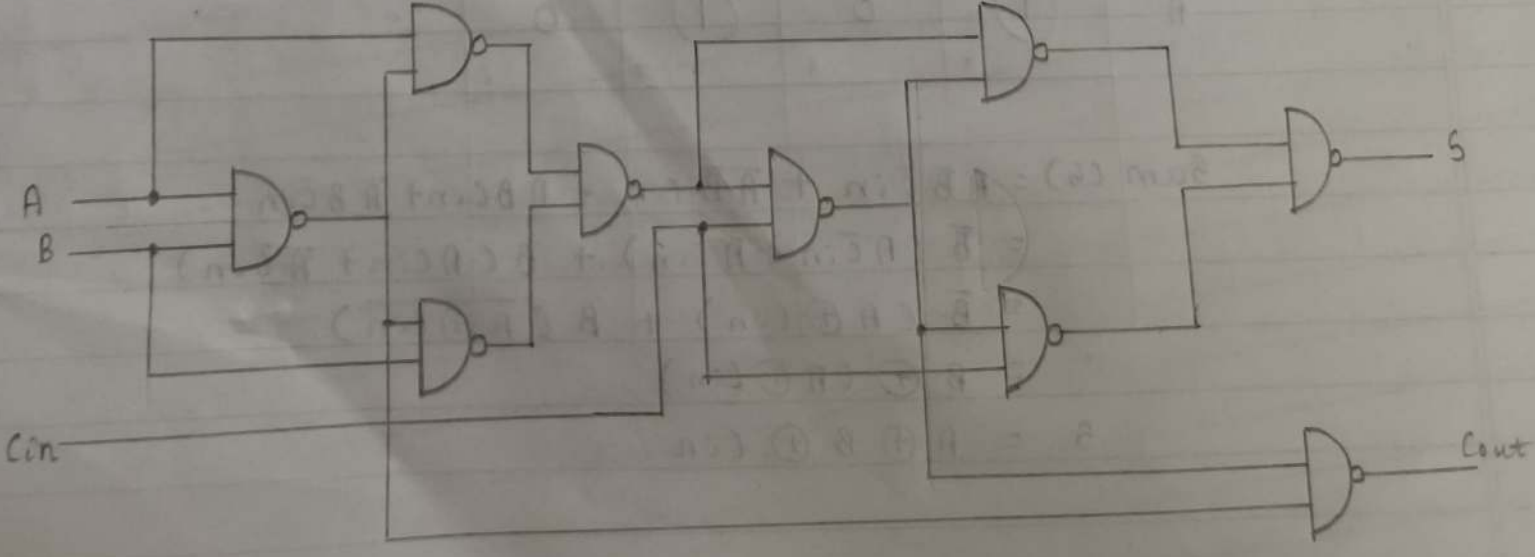

# SPPU-SE-COMP-CONTENT - KSKA Git

ii)

cout

cout

Bein

A

$\bar{B}Cin$

$\bar{B}Cout$

$BCin$

$BCout$

$\bar{A}$

0

1

3

2

A

0

5

7


6

$$cout = AB + ACin + BCin$$



3) Using NOR Gate

# SPPU-SE-COMP-CONTENT - KSKA Git

 

$$Cout = A \cdot B + A \cdot B + B \cdot Cin$$

# SPPU-SE-COMP-CONTENT - KSKA Git

## 2. Full Subtractor

### • Truth Table

A	B	B <sub>in</sub>	D	B <sub>out</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### • K-map

#### i) Difference (D)


		D			
		B <sub>in</sub>			
A	Ā	B̄B <sub>in</sub>	B̄B <sub>in</sub>	BB <sub>in</sub>	B <sub>in</sub>
	A	0	1	0	1
		0	1	3	2
	Ā	0	1	0	1
	A	1	0	1	0
		4	5	7	6

$$\begin{aligned}
 D &= A\bar{B}\bar{B}_{in} + \bar{A}B\bar{B}_{in} + AB\bar{B}_{in} + \bar{A}B\bar{B}_{in} \\
 &= \bar{B}(A\bar{B}_{in} + \bar{A}B_{in}) + B(A\bar{B}_{in} + \bar{A}B_{in}) \\
 &= \bar{B}(A \oplus B_{in}) + B(\overline{A \oplus B_{in}}) \\
 &= B \oplus (A \oplus B_{in}) \\
 &= A \oplus B \oplus B_{in}
 \end{aligned}$$


→ Circuit Diagram

1) Using Basic Gates

# SPPU-SE-COMP-CONTENT - KSKA Git

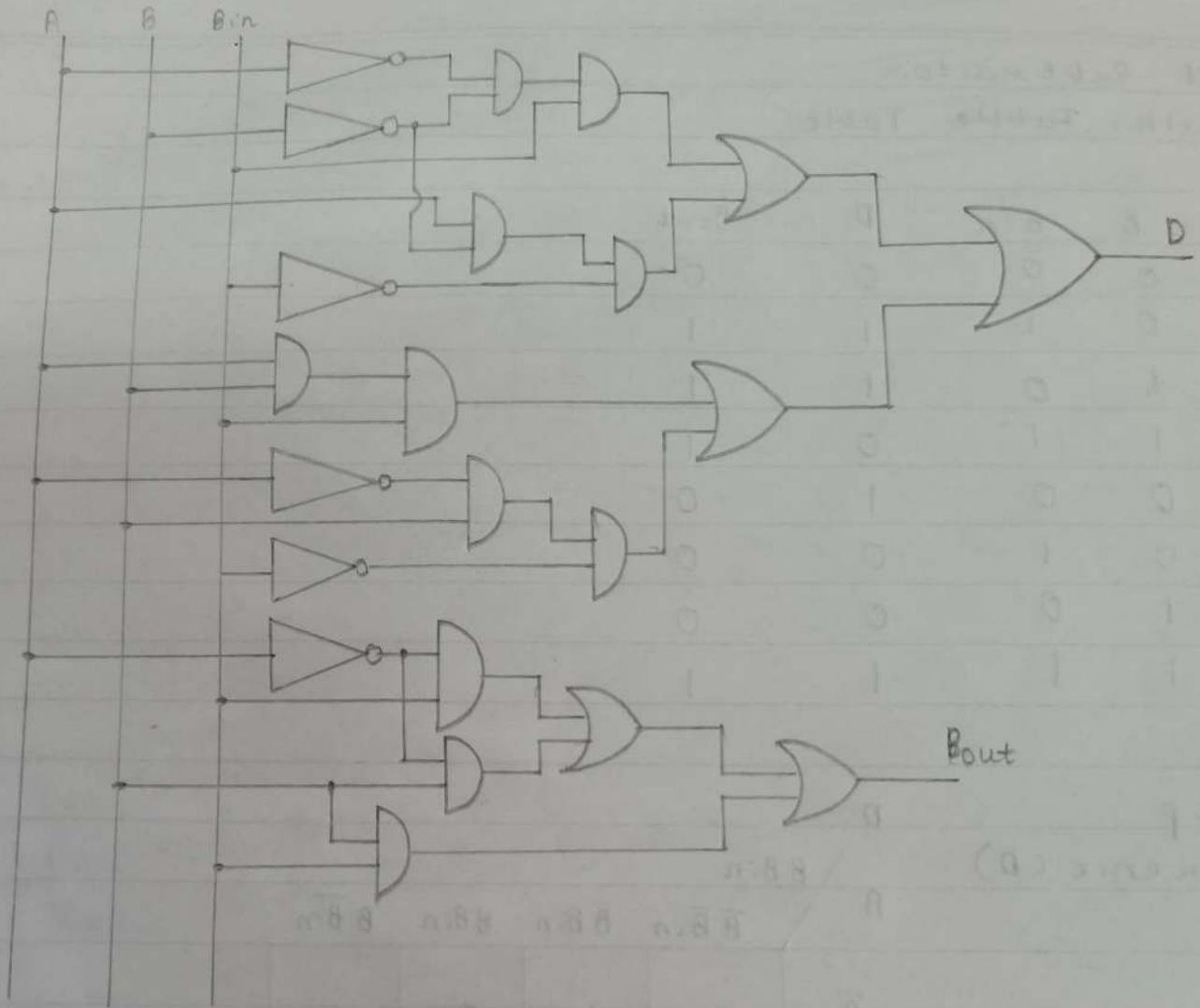

2) Using NAND Gate

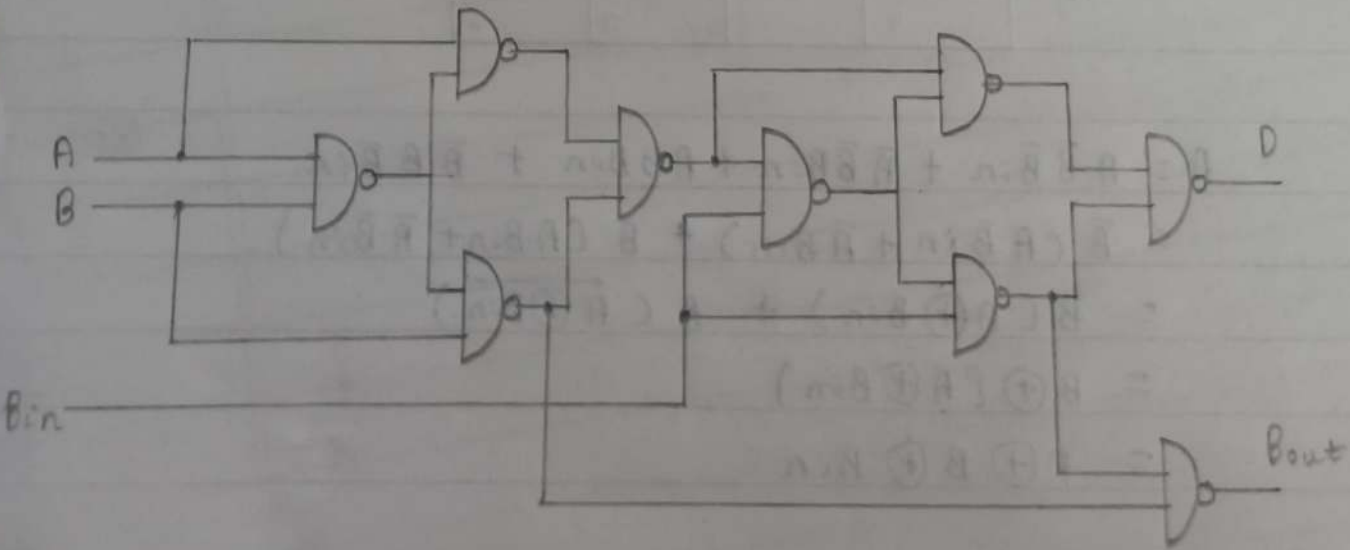

# SPPU-SE-COMP-CONTENT - KSKA Git

ii) Boolean (Bout)

A	$BB_{in}$	$\bar{B}B_{in}$	$B\bar{B}_{in}$	$\bar{B}\bar{B}_{in}$
$\bar{A}$	0 <sub>0</sub>	1 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
A	0 <sub>4</sub>	0 <sub>5</sub>	1 <sub>7</sub>	0 <sub>6</sub>

$$B_{out} = \bar{A}B_{in} + \bar{A}B + B\bar{B}_{in}$$

→ Conclusion:

- Realized Full Adder and Subtractor using Basic and Universal Gates.

3) Using NOR Gate  
SPPU-SE-COMP-CONTENT - KSKA Git

