

# SPPU-SE-COMP-CONTENT - KSKA Git

## Assignment 3

Title: Multiplexer

Problem Statement: Realization of Boolean Expression for suitable combination logic using MUX 74151

Hardware and

software

Requirements:

Theory:

1) What is multiplexer?


- Multiplexer is a combinational circuit that has maximum  $n$  data inputs,  $m$  selection lines and single output line.
- One of these data inputs will be connected to the output based on the values of selection lines.
- Relation between data inputs ( $n$ ) and select inputs ( $m$ ) is  $2^m = n$ .

2) Necessity of Multiplexer:-

- Multiplexing technique is designed to reduce the number of electrical connections or leads on the display matrix.
- Whereas driving signals are applied not to each pixel individually but to a group of rows

# SPPU-SE-COMP-CONTENT - KSKA Git

→ Block diagram

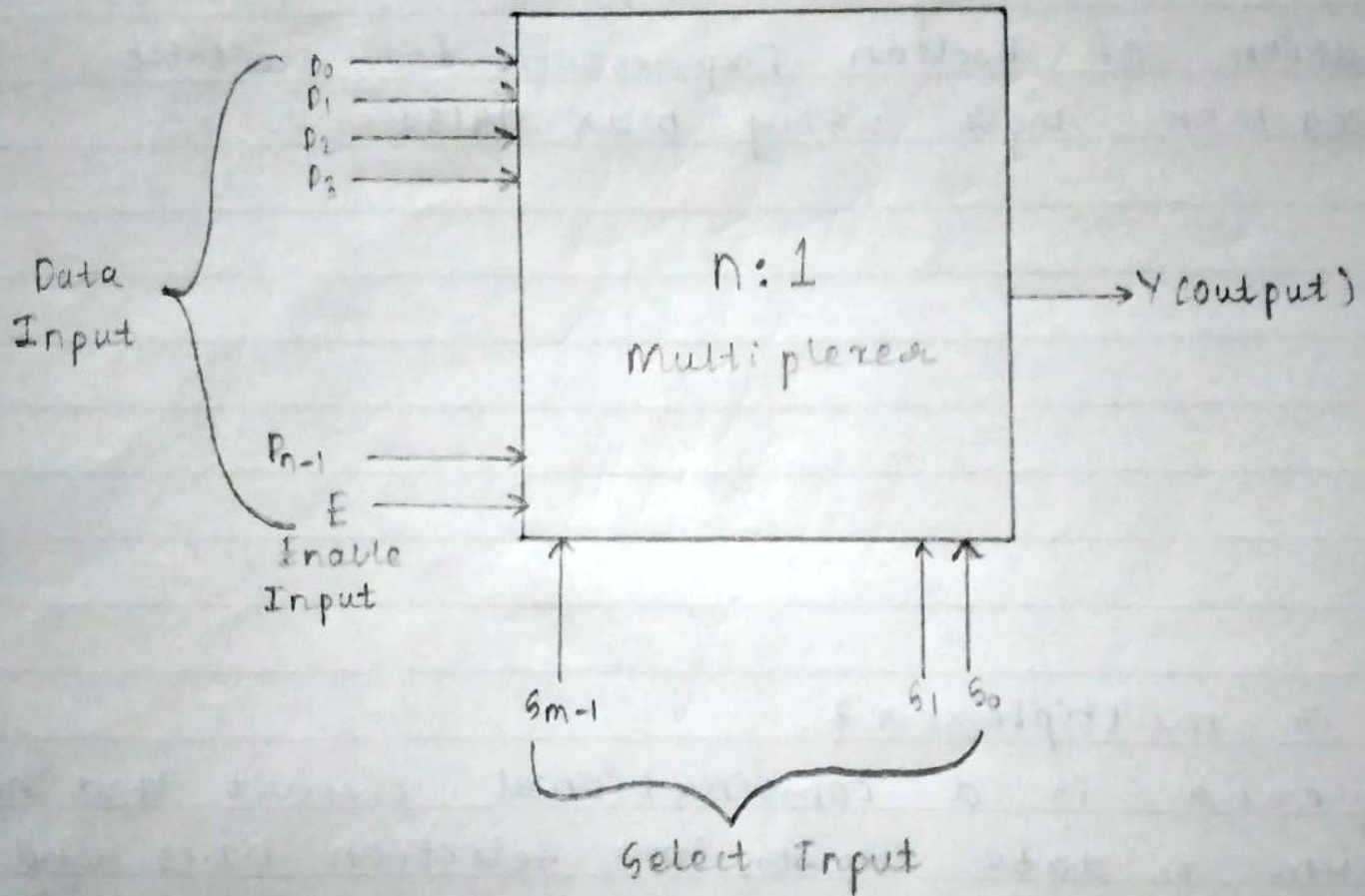



# SPPU-SE-COMP-CONTENT - KSKA Git

and columns at a time.

- Besides reducing the number of individually independent interconnections, multiplexing also simplifies the drive electronics, reduces the cost and provides direct interface with the microprocessors.

## 3) Advantages of multiplexer:-

- In a multiplexer the ~~number~~ usage of number of wires can be decreased.
- It reduces cost as well as complexity of the circuit.
- MUX doesn't require K-map and simplification.
- MUX can be used to implement several combinational circuits.
- The logic design can be simplified through mux.


## 4) Applications of mux:-

- Multiplexer is used as a data selector device.
- Multiplexers are used in communication systems to increase efficiency of the system.
- To maintain large amount of data, multiplexers are used in computer memory systems.
- Multiplexers are also used in PLC (Programmable Logic Control) systems.
- Multiplexers are used in communication systems to increase the efficiency of the system.



# SPPU-SE-COMP-CONTENT – KSKA Git

• Diagram

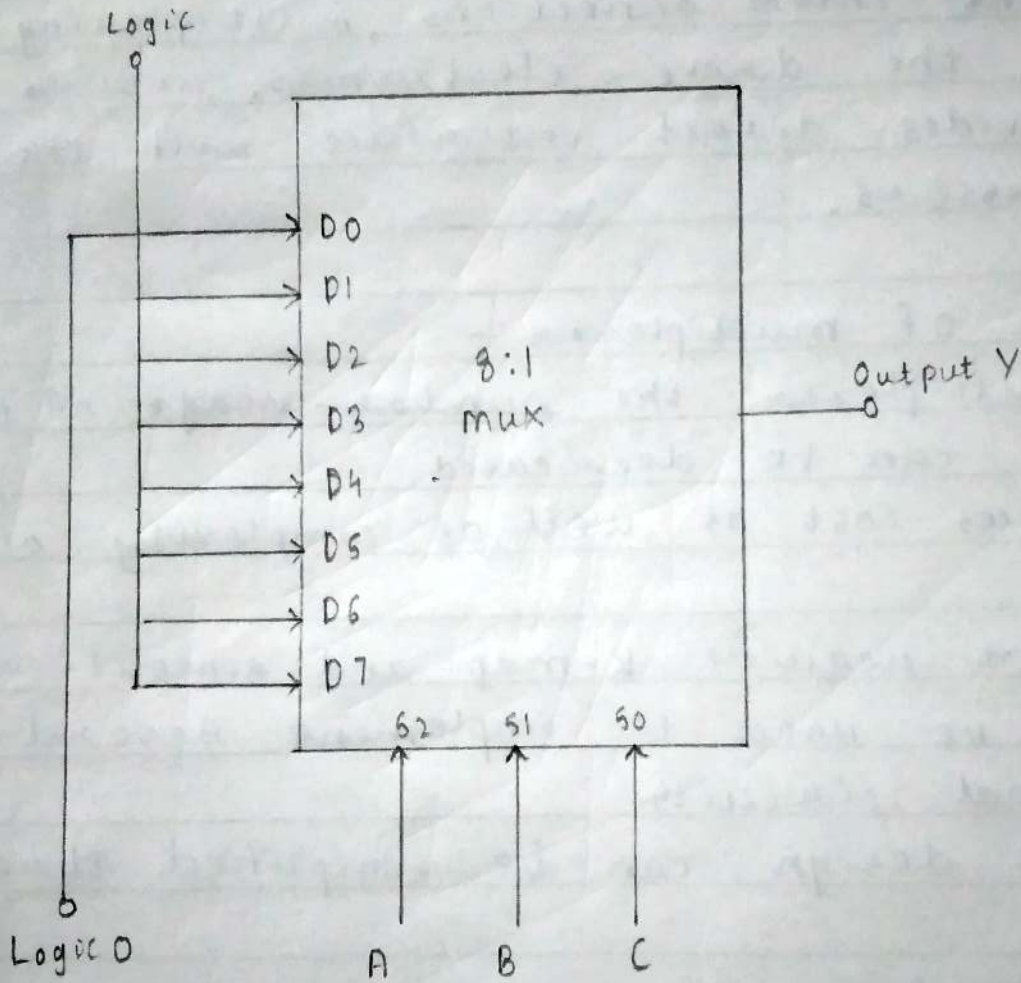

# SPPU-SE-COMP-CONTENT - KSKA Git

Design:

1. Design Boolean Expression using mux

Function = Sum of Product (SOP)  $Y = \sum m(1, 2, 3, 4, 5, 6, 7)$


• Truth table

A	B	C	Y	
0	0	0	0	D0
0	0	1	1	D1
0	1	0	1	D2
0	1	1	1	D3
1	0	0	1	D4
1	0	1	1	D5
1	1	0	1	D6
1	1	1	1	D7



# SPPU-SE-COMP-CONTENT - KSKA Git
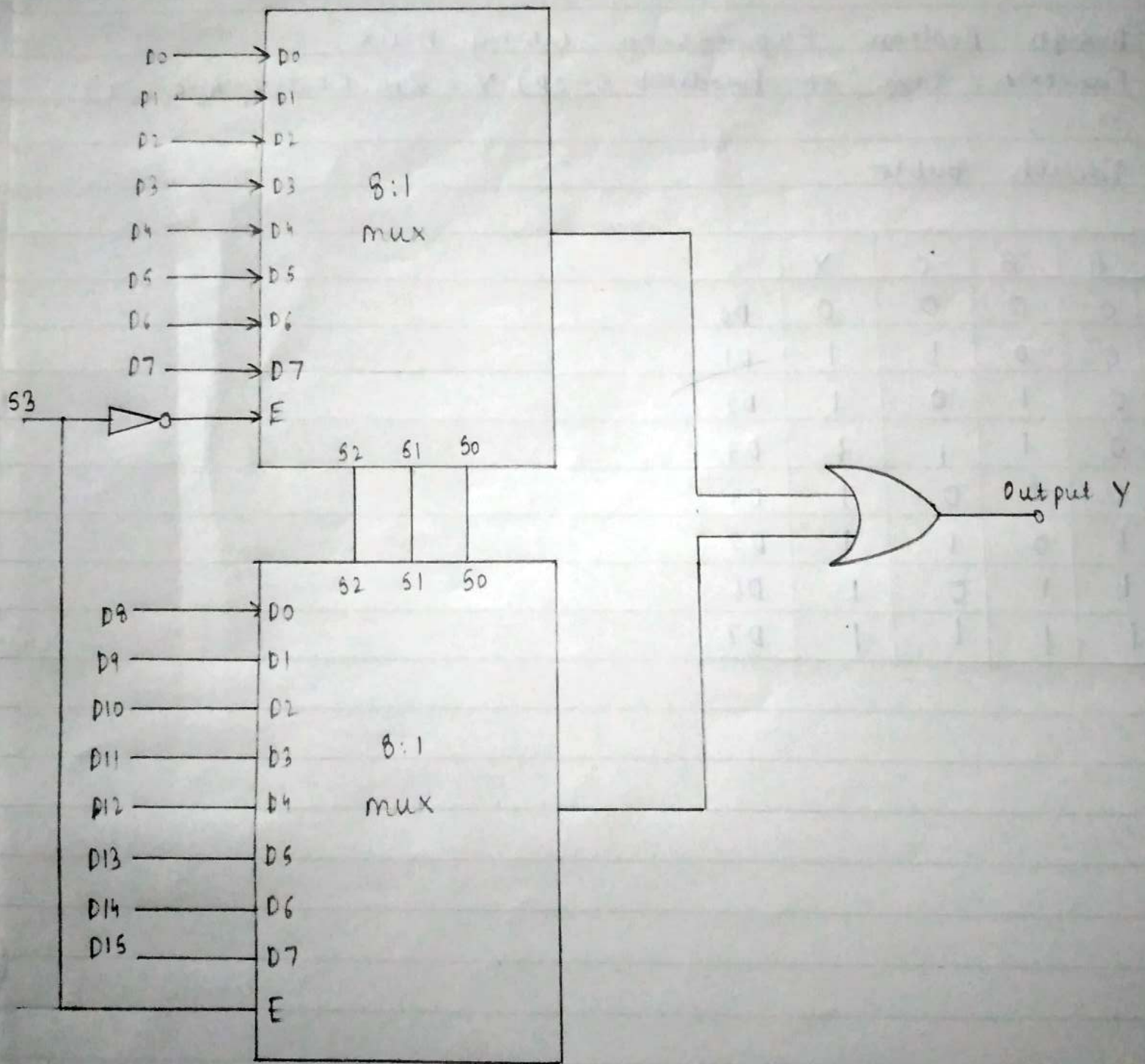
## 2. Implementation of 16:1 mux using 8:1 mux



# SPPU-SE-COMP-CONTENT - KSKA Git

→  $F(A, B, C, D) = \sum m(2, 4, 5, 7, 10, 14)$

- Use hardware reduction method and implement the given Boolean expression with the help of neat logic diagram. (N-circle method).

→ Simplification

- Truth table

	D0	D1	D2	D3	D4	D5	D6	D7
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
I/P to mux	0	0	1	0	$\bar{A}$	$\bar{A}$	A	$\bar{A}$

Conclusion: Realized Boolean Expression for suitable combination logic using mux 74151



• Diagram

# SPPU-SE-COMP-CONTENT - KSKA Git

