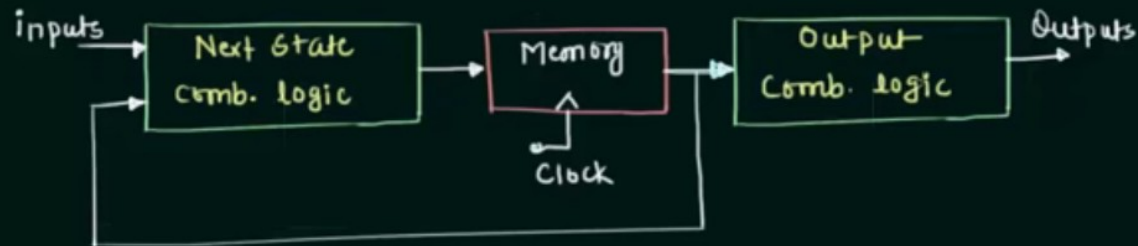


L-14 Mealy and Moore State-2


Mealy and Moore State Machines (Part 2)

Mealy state machine: The output is the function of present state as well as the input.




Mealy and Moore State Machines (Part 2)

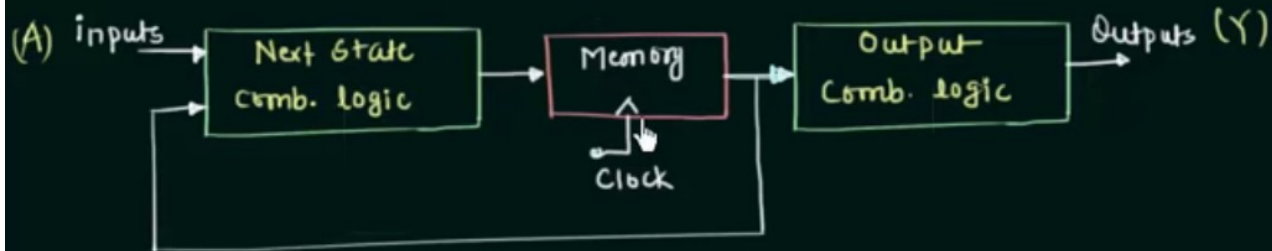Mealy state machine: The output is the function of present state as well as the input.







Mealy and Moore State Machines (Part 2)


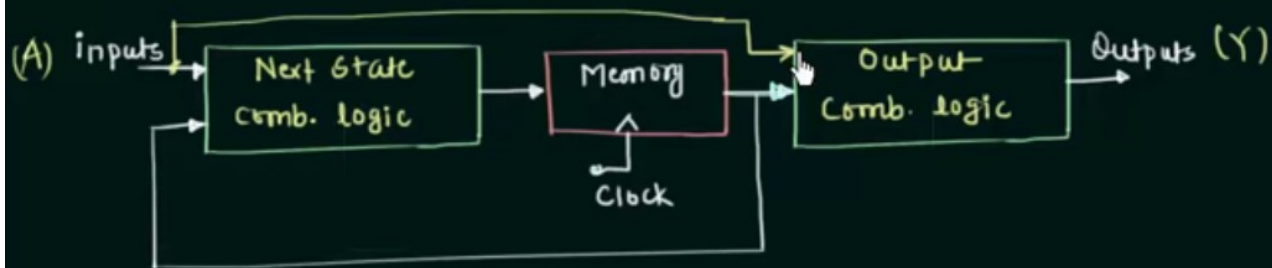
Mealy state machine: The output is the function of present state as well as the input.





Mealy and Moore State Machines (Part 2)

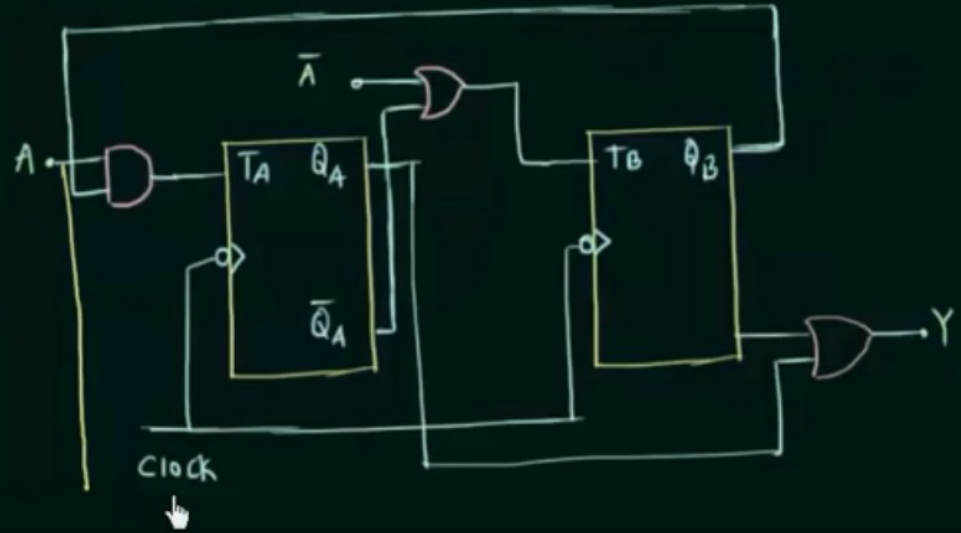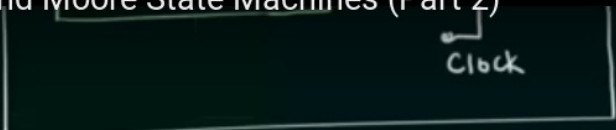

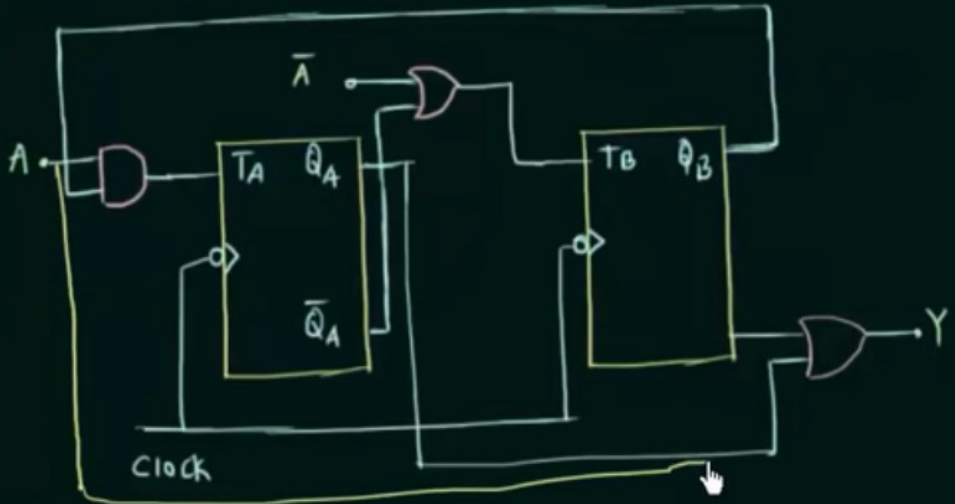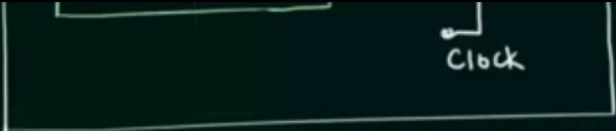


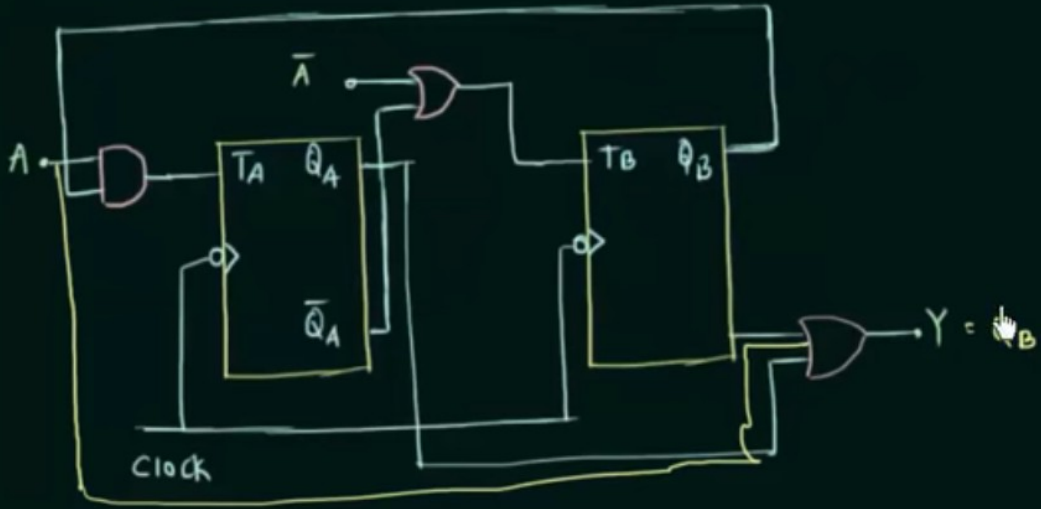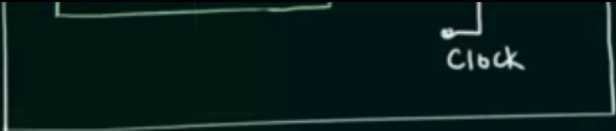

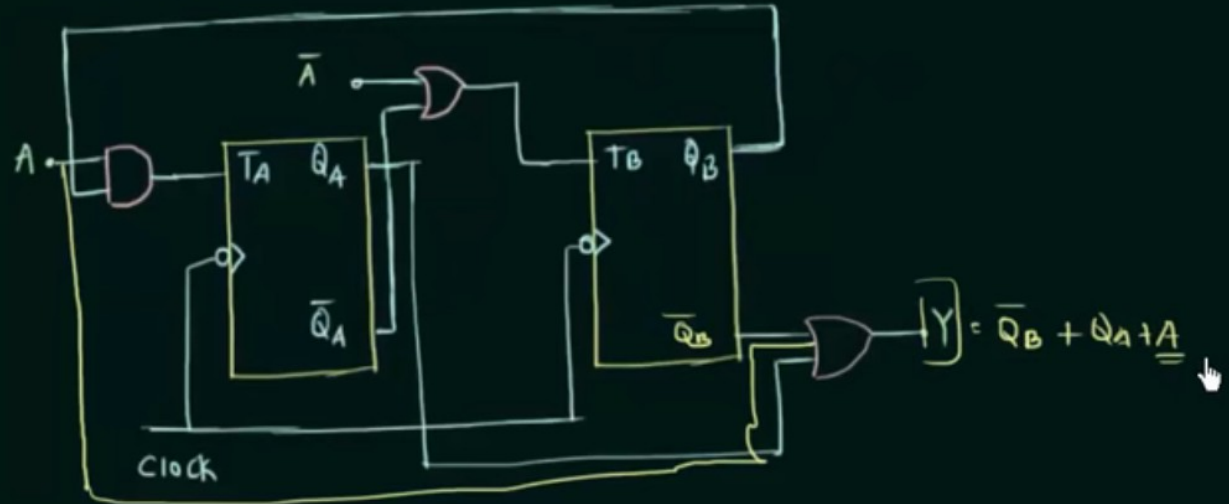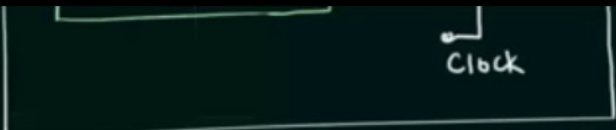

Mealy and Moore State Machines (Part 2)

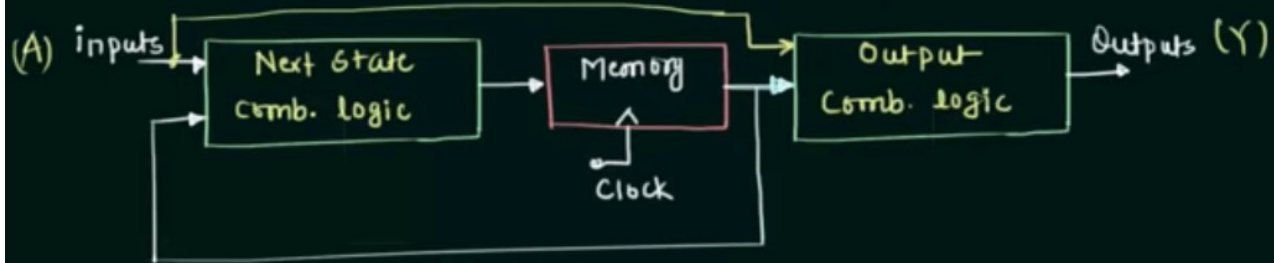
Mealy state machine: The output is the function of present state as well as the input.



Mealy and Moore State Machines (Part 2)

Mealy state machine: The output is the function of present state as well as the input.

Mealy: no of states are less

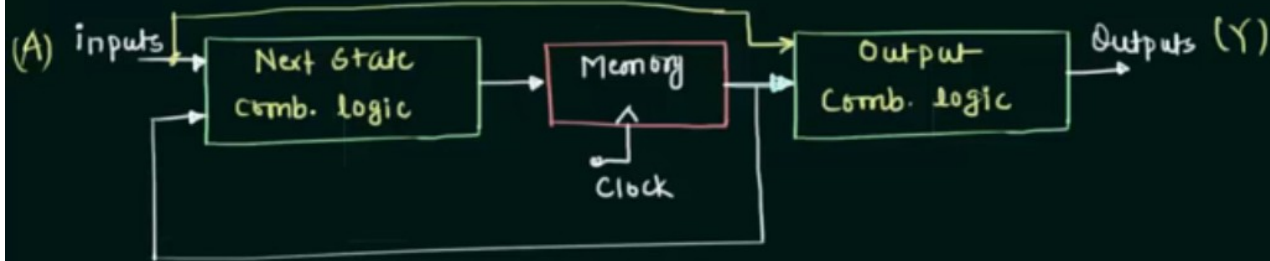

• **Questions????**