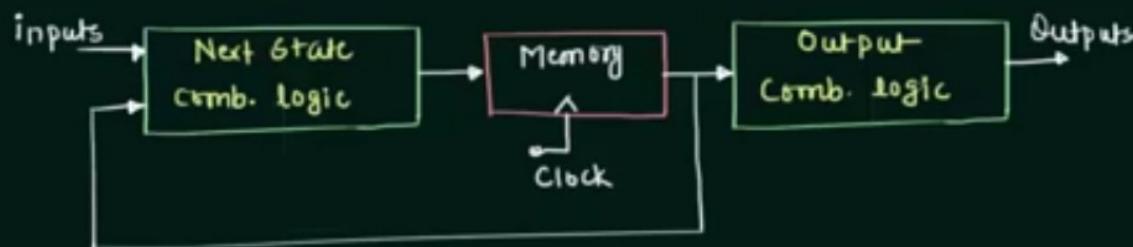


# L-14 Mealy and Moore State Machines-1

## Mealy and Moore State Machines (Part 1)


» There are two models developed for representing synch. sequential circuits:



## Mealy and Moore State Machines (Part 1)

» There are two models developed for representing synch. sequential circuits:

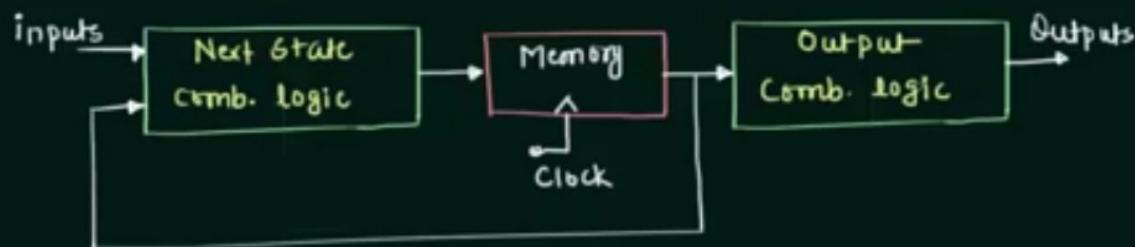- i) Moore Circ / Moore State Mach.
- ii) Mealy Circ / Mealy State Machine




## Mealy and Moore State Machines (Part 1)

» There are two models developed for representing synch. sequential circuits:

i) Moore Circ / Moore State Mach.

ii) Mealy Circ / Mealy State Machine

\* only in the way the o/p is generated

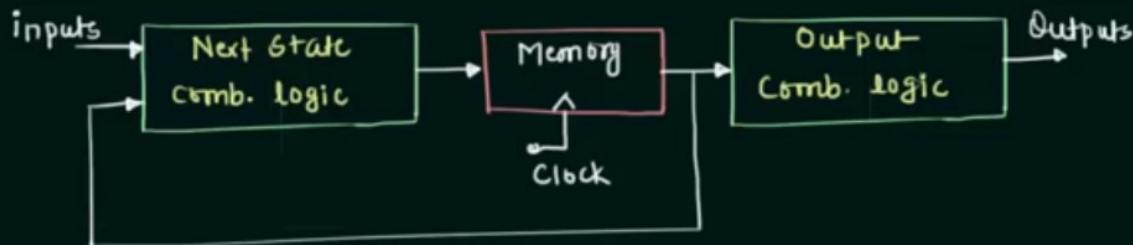


## Mealy and Moore State Machines (Part 1)

» There are two models developed for representing synch. sequential circuits:

i) Moore Circ / Moore State Mach. :- O/P is the fun of P.S. only


ii) Mealy Circ / Mealy State Machine :- O/P is the fun of P.S. as well as I/P



\* only in the way the O/P is generated


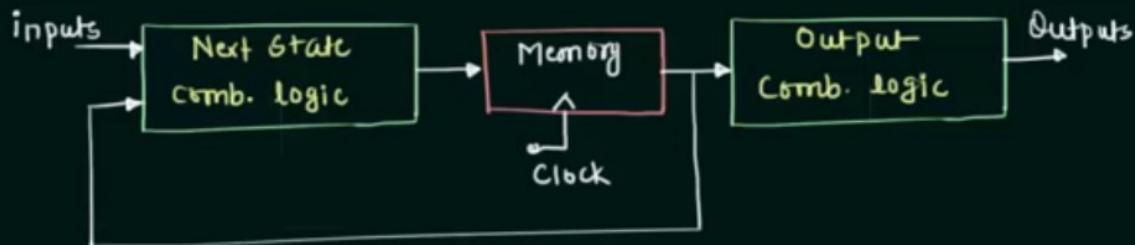


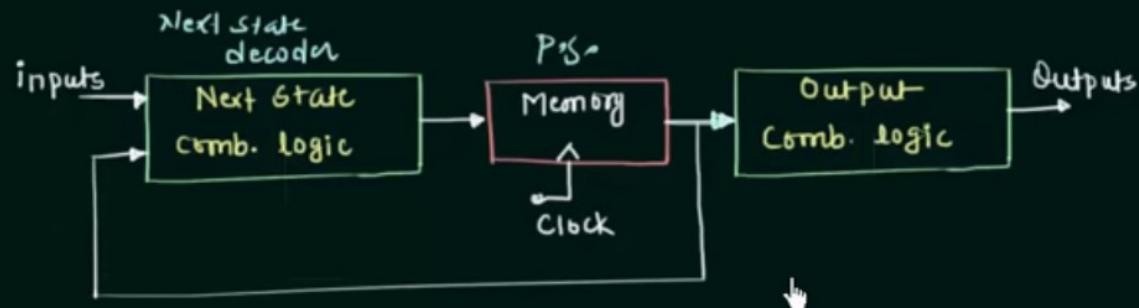i) Mealy or/ Clearable state machine :- Output is a function of present state

- \* only in the way the O/p is generated



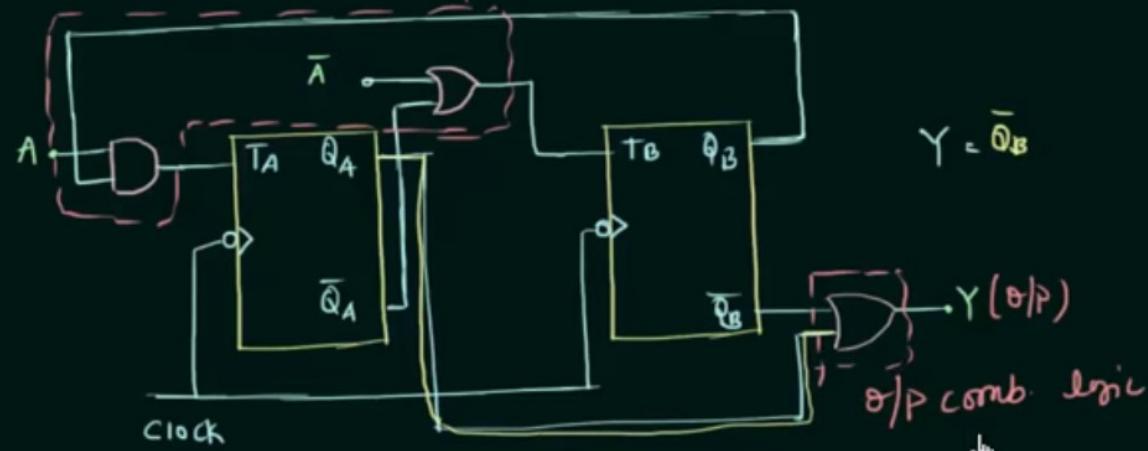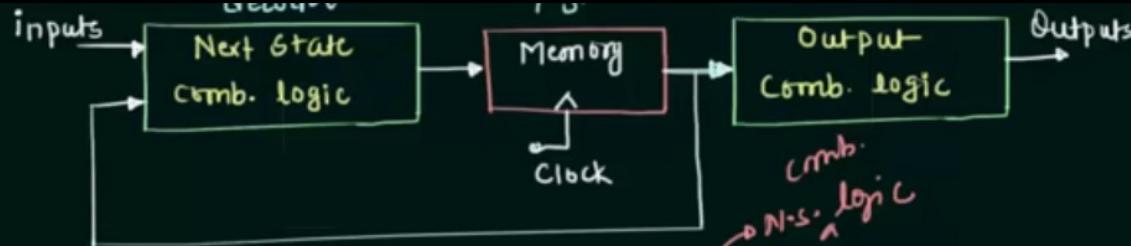

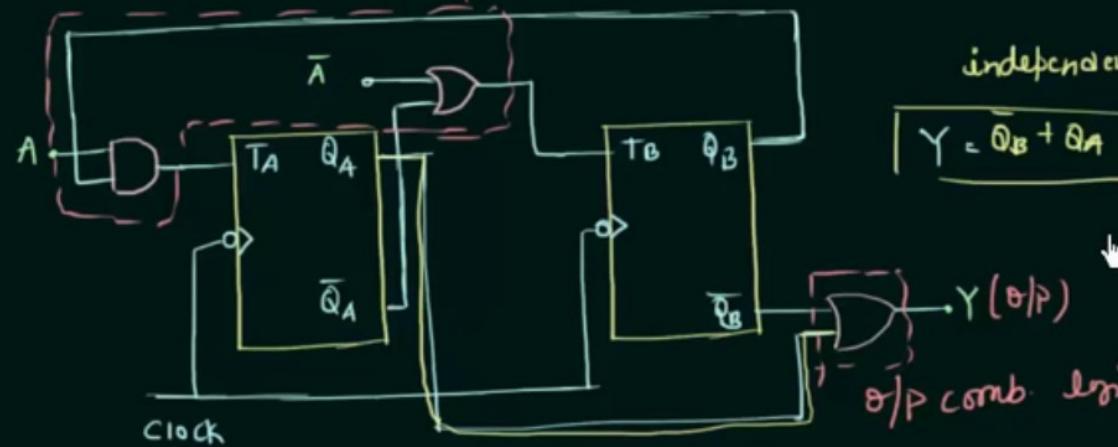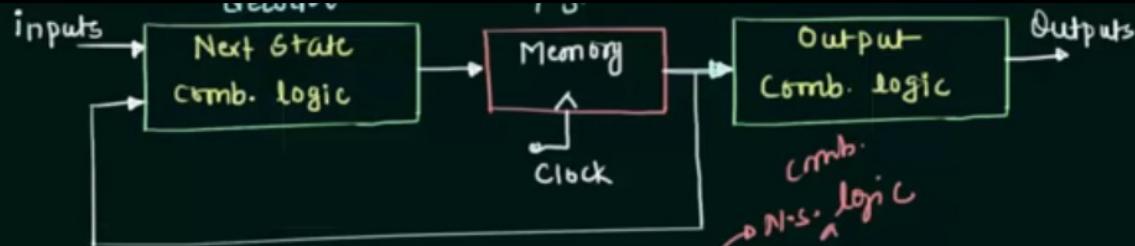

independent of  $A$  (i/p)

$$Y = \bar{Q}_B + Q_A$$



↓

↓

↓

↓

↓

↓

↓

↓

↓


↓

↓

↓



↓







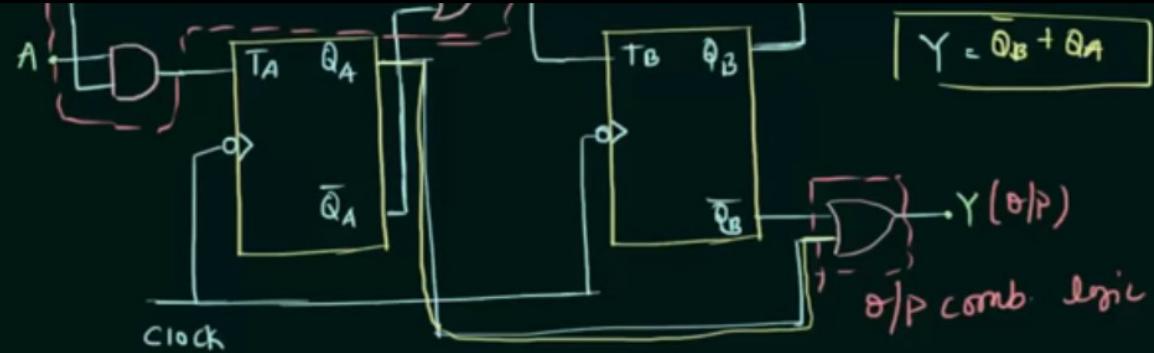


00  
01  
10



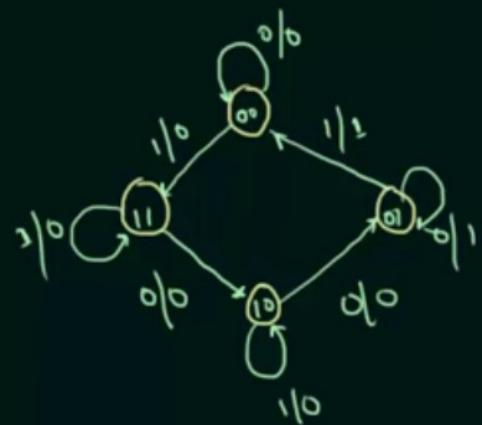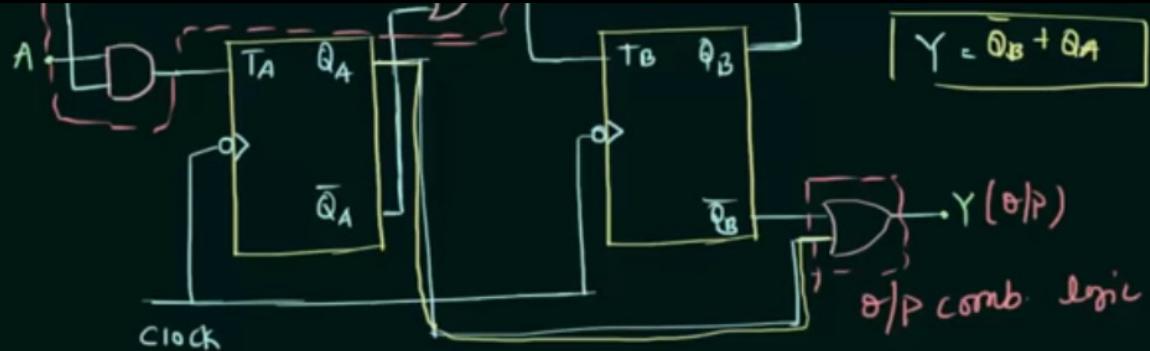

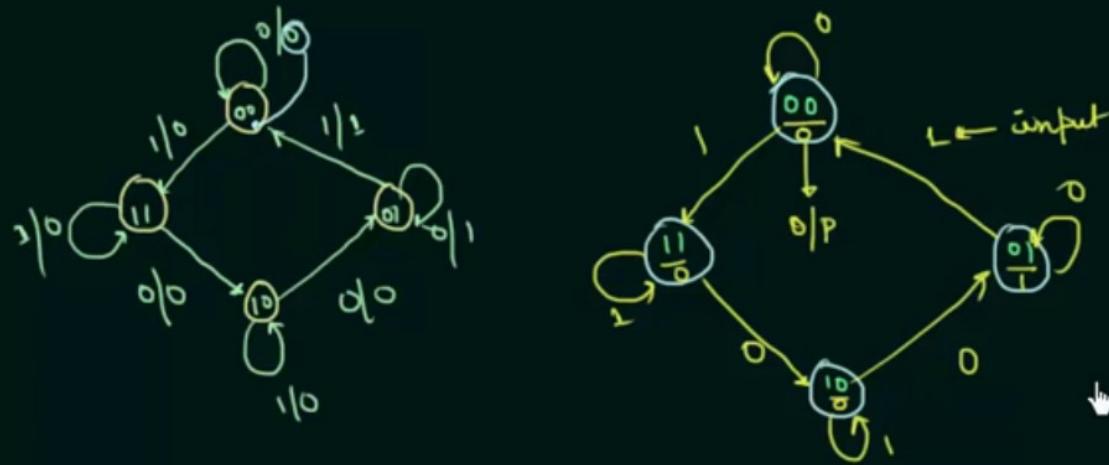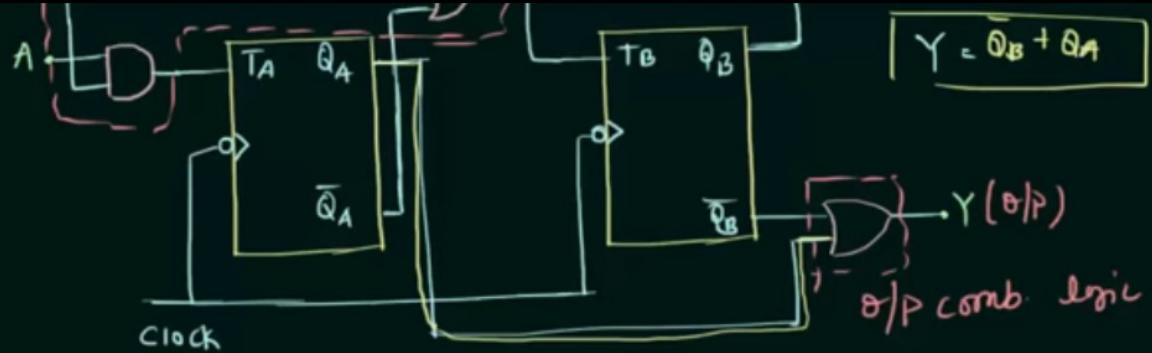

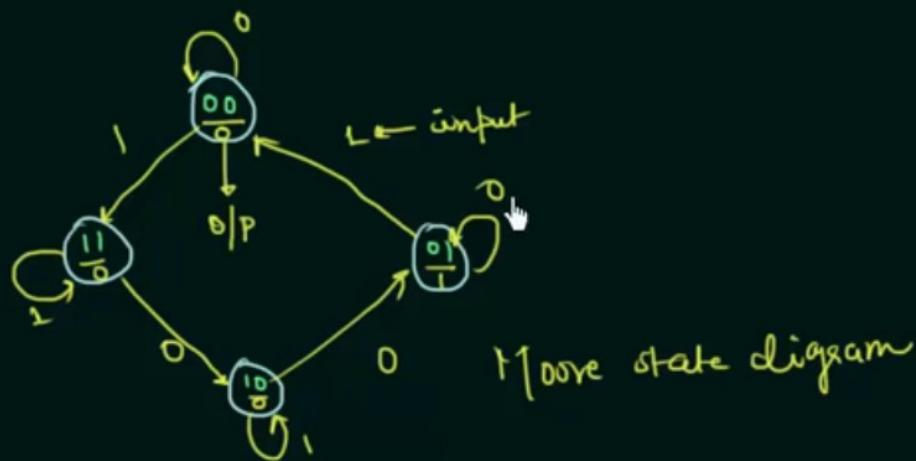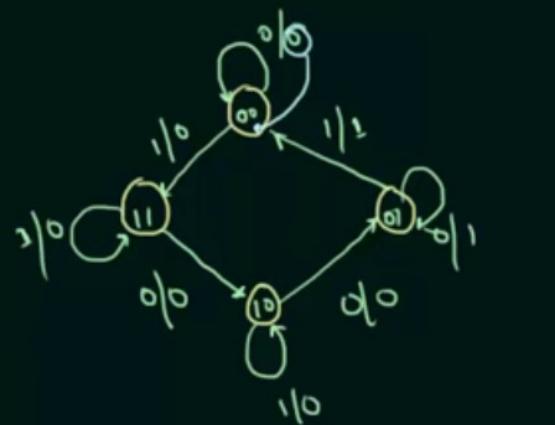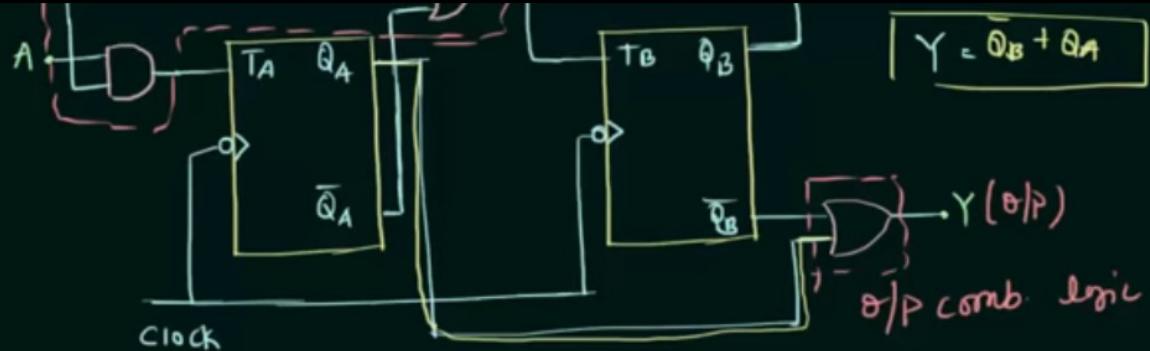

- **Questions???**